

542 ■ Principles of Electronics

Operation. The input signal (V_{in}) is capacitively coupled to the gate terminal. In the absence of the signal, d.c. value of $V_{GS} = 0V$. When signal (V_{in}) is applied, V_{gs} swings above and below its zero value (Q d.c. value of $V_{GS} = 0V$), producing a swing in drain current I_d .

(i) A small change in gate voltage produces a large change in drain current as in a *JFET*. This fact makes *MOSFET* capable of raising the strength of a weak signal; thus acting as an amplifier.

(ii) During the positive half-cycle of the signal, the positive voltage on the gate increases and produces the enhancement-mode. This increases the channel conductivity and hence the drain current.

(iii) During the negative half-cycle of the signal, the positive voltage on the gate decreases and produces depletion-mode. This decreases the conductivity and hence the drain current.

The result of above action is that a small change in gate voltage produces a large change in the drain current. This large variation in drain current produces a large a.c. output voltage across drain resistance R_D . In this way, *D-MOSFET* acts as an amplifier. Fig. 19.53 shows the amplifying action of *D-MOSFET* on transconductance curve.

Voltage gain. The a.c. analysis of *D-MOSFET* is similar to that of the *JFET*. Therefore, voltage gain expressions derived for *JFET* are also applicable to *D-MOSFET*.

$$\begin{aligned} \text{Voltage gain, } A_v &= g_m R_D && \dots \text{ for unloaded } D\text{-MOSFET amplifier} \\ &= g_m R_{AC} && \dots \text{ for loaded } D\text{-MOSFET amplifier} \end{aligned}$$

Note the total a.c. drain resistance $R_{AC} = R_D \parallel R_L$.

Example 19.33. The *D-MOSFET* used in the amplifier of Fig. 19.54 has an $I_{DSS} = 12 \text{ mA}$ and $g_m = 3.2 \text{ mS}$. Determine (i) d.c. drain-to-source voltage V_{DS} and (ii) a.c. output voltage. Given $v_{in} = 500 \text{ mV}$.

 


Fig. 19.54

Solution.

(i) Since the amplifier is zero biased, $I_D = I_{DSS} = 12 \text{ mA}$.

$$\begin{aligned} \therefore V_{DS} &= V_{DD} - I_{DSS} R_D \\ &= 15V - (12 \text{ mA}) (0.62 \text{ k}\Omega) = \mathbf{7.56V} \end{aligned}$$

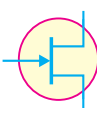

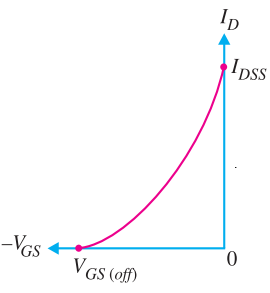
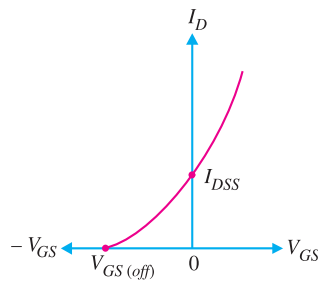
(ii) Total a.c. drain resistance R_{AC} of the circuit is

$$R_{AC} = R_D \parallel R_L = 620\Omega \parallel 8.2 \text{ k}\Omega = 576\Omega$$

$$\begin{aligned} \therefore v_{out} &= A_v \times v_{in} = (g_m R_{AC}) (v_{in}) \\ &= (3.2 \times 10^{-3} \text{ S} \times 576 \Omega) (500 \text{ mV}) = \mathbf{922 \text{ mV}} \end{aligned}$$

19.35 D-MOSFETs Versus JFETs

Table below summarises many of the characteristics of *JFETs* and *D-MOSFETs*.

| Devices: | JFETs | D-MOSFETs |
|------------------------------|---|--|
| Schematic symbol: |  |  |
| Transconductance curve: |  |  |
| Modes of operation: | Depletion only | Depletion and enhancement |
| Commonly used bias circuits: | Gate bias Self bias Voltage-divider bias | Gate bias Self bias Voltage-divider bias Zero bias |
| Advantages: | Extremely high input impedance. | Higher input impedance than a comparable <i>JFET</i> . Can operate in both modes (depletion and enhancement). |
| Disadvantages: | Bias instability. Can operate only in the depletion mode. | Bias instability. More sensitive to changes in temperature than the <i>JFET</i> . |

19.36 E-MOSFET

Two things are worth noting about *E-MOSFET*. First, *E-MOSFET* operates *only* in the enhancement mode and has no depletion mode. Secondly, the *E-MOSFET* has no physical channel from source to drain because the substrate extends completely to the SiO_2 layer [See Fig. 19.55 (i)]. It is only by the application of V_{GS} (gate-to-source voltage) of proper magnitude and polarity that the device starts conducting. The minimum value of V_{GS} of proper polarity that turns on the *E-MOSFET* is called **Threshold voltage** [$V_{GS(th)}$]. The *n*-channel device requires positive $V_{GS} (\geq V_{GS(th)})$ and the *p*-channel device requires negative $V_{GS} (\leq V_{GS(th)})$.

Operation. Fig. 19.55 (i) shows the circuit of *n*-channel *E-MOSFET*. The circuit action is as under :

(i) When $V_{GS} = 0\text{V}$ [See Fig. 19.55(i)], there is no channel connecting the source and drain. The *p* substrate has only a few thermally produced free electrons (minority carriers) so that drain current is essentially zero. For this reason, *E-MOSFET* is normally *OFF* when $V_{GS} = 0\text{V}$. Note that this behaviour of *E-MOSFET* is quite different from *JFET* or *D-MOSFET*.

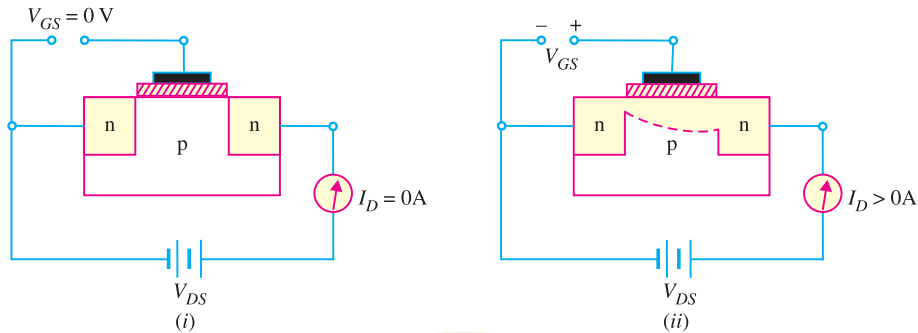


Fig. 19.55

(ii) When gate is made positive (i.e. V_{GS} is positive) as shown in Fig. 19.55 (ii), it attracts free electrons into the p region. The free electrons combine with the holes next to the SiO_2 layer. If V_{GS} is positive enough, all the holes touching the SiO_2 layer are filled and free electrons begin to flow from the source to drain. The effect is the same as creating a thin layer of n -type material (i.e. inducing a thin n -channel) adjacent to the SiO_2 layer. Thus the E -MOSFET is turned ON and drain current I_D starts flowing from the source to the drain.

The minimum value of V_{GS} that turns the E -MOSFET ON is called **threshold voltage** [$V_{GS(th)}$].

(iii) When V_{GS} is less than $V_{GS(th)}$, there is no induced channel and the drain current I_D is zero. When V_{GS} is equal to $V_{GS(th)}$, the E -MOSFET is turned ON and the induced channel conducts drain current from the source to the drain. Beyond $V_{GS(th)}$, if the value of V_{GS} is increased, the newly formed channel becomes wider, causing I_D to increase. If the value of V_{GS} decreases [not less than $V_{GS(th)}$], the channel becomes narrower and I_D will decrease. This fact is revealed by the transconductance curve of n -channel E -MOSFET shown in Fig. 19.56. As you can see, $I_D = 0$ when $V_{GS} = 0$. Therefore, the value of I_{DSS} for the E -MOSFET is zero. Note also that there is no drain current until V_{GS} reaches $V_{GS(th)}$.

 


Fig. 19.56

 


Fig. 19.57

Schematic Symbols. Fig. 19.57 (i) shows the schematic symbols for n -channel E -MOSFET whereas Fig. 19.57 (ii) shows the schematic symbol for p -channel E -MOSFET. When $V_{GS} = 0$, the E -MOSFET is OFF because there is no conducting channel between source and drain. The broken channel line in the symbols indicates the normally OFF condition.

Equation for Transconductance Curve. Fig. 19.58 shows the transconductance curve for n -channel E -MOSFET. Note that this curve is different from the transconductance curve for n -channel JFET or n -channel D-MOSFET. It is because it starts at $V_{GS(th)}$ rather than $V_{GS(off)}$ on the horizontal axis and never intersects the vertical axis. The equation for the E -MOSFET transconductance curve (for $V_{GS} > V_{GS(th)}$) is

$$I_D = K (V_{GS} - V_{GS(th)})^2$$

The constant K depends on the particular E -MOSFET and its value is determined from the following equation :

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$

Any data sheet for an E -MOSFET will include the current $I_{D(on)}$ and the voltage $V_{GS(on)}$ for one point well above the threshold voltage as shown in Fig. 19.58.

 


Fig. 19.58

Example 19.34. The data sheet for an E -MOSFET gives $I_{D(on)} = 500 \text{ mA}$ at $V_{GS} = 10\text{V}$ and $V_{GS(th)} = 1\text{V}$. Determine the drain current for $V_{GS} = 5\text{V}$.

Solution. Here $V_{GS(on)} = 10 \text{ V}$.

$$I_D = K (V_{GS} - V_{GS(th)})^2 \quad \dots (i)$$

$$\text{Here} \quad K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2} = \frac{500 \text{ mA}}{(10\text{V} - 1\text{V})^2} = 6.17 \text{ mA/V}^2$$

Putting the various values in eq. (i), we have,

$$I_D = 6.17 (5\text{V} - 1\text{V})^2 = \mathbf{98.7 \text{ mA}}$$

Example 19.35. The data sheet for an E -MOSFET gives $I_{D(on)} = 3 \text{ mA}$ at $V_{GS} = 10\text{V}$ and $V_{GS(th)} = 3\text{V}$. Determine the resulting value of K for the device. How will you plot the transconductance curve for this MOSFET ?

Solution. The value of K can be determined from the following equation :

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$

$$\text{Here} \quad I_{D(on)} = 3 \text{ mA} ; V_{GS(on)} = 10\text{V} ; V_{GS(th)} = 3\text{V}$$

$$\therefore K = \frac{3 \text{ mA}}{(10\text{V} - 3\text{V})^2} = \frac{3 \text{ mA}}{(7\text{V})^2} = \mathbf{0.061 \times 10^{-3} \text{ A/V}^2}$$

$$\text{Now} \quad I_D = K (V_{GS} - V_{GS(th)})^2$$

In order to plot the transconductance curve for the device, we shall determine a few points for the curve by changing the value of V_{GS} and noting the corresponding values of I_D .

$$\text{For } V_{GS} = 5\text{V} ; I_D = 0.061 \times 10^{-3} (5\text{V} - 3\text{V})^2 = 0.244 \text{ mA}$$

$$\text{For } V_{GS} = 8\text{V} ; I_D = 0.061 \times 10^{-3} (8\text{V} - 3\text{V})^2 = 1.525 \text{ mA}$$

$$\text{For } V_{GS} = 10\text{V} ; I_D = 0.061 \times 10^{-3} (10\text{V} - 3\text{V})^2 = 3 \text{ mA}$$

$$\text{For } V_{GS} = 12\text{V} ; I_D = 0.061 \times 10^{-3} (12\text{V} - 3\text{V})^2 = 4.94 \text{ mA}$$

Thus we can plot the transconductance curve for the E -MOSFET from these V_{GS}/I_D points.

19.37 E-MOSFET Biasing Circuits

One of the problems with E -MOSFET is the fact that many of the biasing circuits used for $JFET$ s and D -MOSFETs cannot be used with this device. For example, E -MOSFETs must have V_{GS} greater than the threshold value ($V_{GS(th)}$) so that zero bias cannot be used. However, there are two popular methods for E -MOSFET biasing viz.

(i) Drain-feedback bias

(ii) Voltage-divider bias

(i) **Drain-feedback bias.** This method of E -MOSFET bias is equivalent to collector-feedback bias in transistors. Fig. 19.59 (i) shows the drain-feedback bias circuit for n -channel E -MOSFET. A

546 ■ Principles of Electronics

high resistance R_G is connected between the drain and the gate. Since the gate resistance is superhigh, no current will flow in the gate circuit (*i.e.* $I_G = 0$). Therefore, there will be no voltage drop across R_G . Since there is no voltage drop across R_G , the gate will be at the same potential as the drain. This fact is illustrated in the d.c. equivalent circuit of drain-feedback bias as in Fig. 19.59 (ii).

$$\therefore V_D = V_G \text{ and } V_{DS} = V_{GS}$$

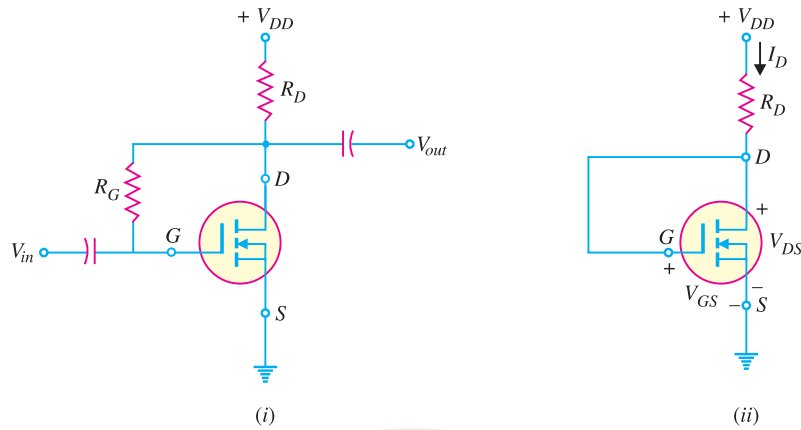


Fig. 19.59

The value of drain-source voltage V_{DS} for the drain-feedback circuit is

$$V_{DS} = V_{DD} - I_D R_D$$

$$\text{Since } V_{DS} = V_{GS}, V_{GS} = V_{DD} - I_D R_D$$

$$\text{Since in this circuit } V_{DS} = V_{GS}; I_D = I_{D(on)}.$$

Therefore, the Q -point of the circuit stands determined.

(ii) Voltage-divider Bias. Fig. 19.60 shows voltage divider biasing arrangement for n -channel E -MOSFET. Since $I_G = 0$, the analysis of the method is as follows :

$$V_{GS} = \frac{V_{DD}}{R_1 + R_2} \times R_2$$

and

$$V_{DS} = V_{DD} - I_D R_D$$

where

$$I_D = K (V_{GS} - V_{GS(th)})^2$$

Once I_D and V_{DS} are known, all the remaining quantities of the circuit such as V_D etc. can be determined.

Example 19.36. Determine V_{GS} and V_{DS} for the E -MOSFET circuit in Fig. 19.61. The data sheet for this particular MOSFET gives $I_{D(on)} = 500 \text{ mA}$ at $V_{GS} = 10 \text{ V}$ and $V_{GS(th)} = 1 \text{ V}$.

Solution. Referring to the circuit shown in Fig. 19.61, we have,

$$\begin{aligned} V_{GS} &= \frac{V_{DD}}{R_1 + R_2} \times R_2 \\ &= \frac{24 \text{ V}}{(100 + 15) \text{ k}\Omega} \times 15 \text{ k}\Omega = 3.13 \text{ V} \end{aligned}$$

The value of K can be determined from the following equation :

 


Fig. 19.60

 


Fig. 19.61

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$

$$= \frac{500 \text{ mA}}{(10\text{V} - 1\text{V})^2} = 6.17 \text{ mA/V}^2 \quad [\text{Q } V_{GS(on)} = 10\text{V}]$$

$$\therefore I_D = K (V_{GS} - V_{GS(th)})^2 = 6.17 \text{ mA/V}^2 (3.13\text{V} - 1\text{V})^2 = 28 \text{ mA}$$

$$\therefore V_{DS} = V_{DD} - I_D R_D = 24\text{V} - (28 \text{ mA}) (470\Omega) = \mathbf{10.8\text{V}}$$

Example 19.37. Determine the values of I_D and V_{DS} for the circuit shown in Fig. 19.62. The data sheet for this particular MOSFET gives $I_{D(on)} = 10 \text{ mA}$ when $V_{GS} = V_{DS}$.

 


Fig. 19.62

Solution. Since in the drain-feedback circuit $V_{GS} = V_{DS}$,

$$\therefore I_D = I_{D(on)} = \mathbf{10 \text{ mA}}$$

The value of V_{DS} (and thus V_{GS}) is given by ;

$$V_{DS} = V_{DD} - I_D R_D$$

$$= 20\text{V} - (10 \text{ mA}) (1 \text{ k}\Omega) = 20\text{V} - 10\text{V} = \mathbf{10\text{V}}$$

Example 19.38. Determine the value of I_D for the circuit shown in Fig. 19.63. The data sheet for this particular MOSFET gives $I_{D(on)} = 10 \text{ mA}$ at $V_{GS} = 10 \text{ V}$ and $V_{GS(th)} = 1.5 \text{ V}$.

 


Fig. 19.63

548 ■ Principles of Electronics

Solution. The value of K can be determined from the following equation :





$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$
$$= \frac{10 \text{ mA}}{(10 \text{ V} - 1.5 \text{ V})^2} = 1.38 \times 10^{-1} \text{ mA/V}^2 \quad [\text{Q } V_{GS(on)} = 10 \text{ V}]$$

From the circuit, the source voltage is seen to be 0V. Therefore, $V_{GS} = V_G - V_S = V_G - 0 = V_G$. The value of $V_G (= V_{GS})$ is given by ;

$$V_G \text{ (or } V_{GS}) = \frac{V_{DD}}{R_1 + R_2} \times R_2 = \frac{10 \text{ V}}{(1 + 1) \text{ M}\Omega} \times 1 \text{ M}\Omega = 5 \text{ V}$$
$$\therefore I_D = K (V_{GS} - V_{GS(th)})^2$$
$$= (1.38 \times 10^{-1} \text{ mA/V}^2) (5 \text{ V} - 1.5 \text{ V})^2 = \mathbf{1.69 \text{ mA}}$$

19.38 D-MOSFETs Versus E-MOSFETs

Table below summarises many of the characteristics of *D-MOSFETs* and *E-MOSFETs*
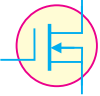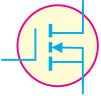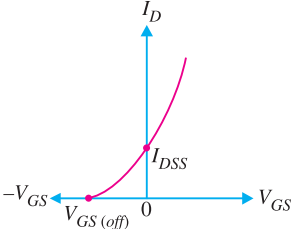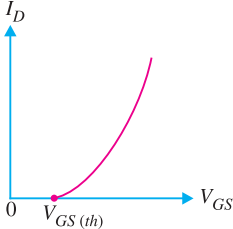
| Devices: | D-MOSFETs | E-MOSFETs |
|------------------------------|---|--|
| Schematic symbol: |  |  |
| Transconductance curve: |  |  |
| Modes of operation: | Depletion and enhancement. | Enhancement only. |
| Commonly used bias circuits: | Gate bias Self bias Voltage-divider bias Zero bias | Gate bias Voltage-divider bias Drain-feedback bias |

MULTIPLE-CHOICE QUESTIONS

1. A *JFET* has three terminals, namely

 - (i) cathode, anode, grid
 - (ii) emitter, base, collector
 - (iii) source, gate, drain
 - (iv) none of the above

2. A *JFET* is similar in operation to valve.
- (i) diode
 - (ii) pentode
 - (iii) triode
 - (iv) tetrode

3. A *JFET* is also called transistor.

 - (i) unipolar
 - (ii) bipolar
 - (iii) unijunction
 - (iv) none of the above

4. A *JFET* is a driven device.